



**BUDAPEST UNIVERSITY OF TECHNOLOGY AND ECONOMICS**  
**FACULTY OF ELECTRICAL ENGINEERING AND INFORMATICS**  
**DEPARTMENT OF MEASUREMENT AND INFORMATION SYSTEMS**

# **Brief Introduction to Verilog HDL**

## **(Part 2)**

**Tamás Raikovich**  
**BUTE DMIS**



# Implementing combinational logic

- Wire type signals can implement combinational logic only
- Reg type signals can implement both combinational and sequential logic
- When combinational logic is implemented using reg type signals:
  - The assignment(s) must be evaluated when at least one input signal is changed:
    - The sensitivity list of the always block has to contain all input signals of the combinational logic or a \* character
    - **negedge** or **posedge** isn't required in the sensitivity list




# Implementing combinational logic

- When combinational logic is implemented using reg type signals:
  - The always blocks must contain fully specified IF and CASE instructions
  - If the IF/CASE instructions are not fully specified, **latches** will be inserted (asynchronous flip-flop)
    - The state of the reg type signal is preserved by the latch when no assignment is made

```
reg reg_signal;
```

 
```
always @(*)  
    if (sel)  
        reg_signal <= in0;
```


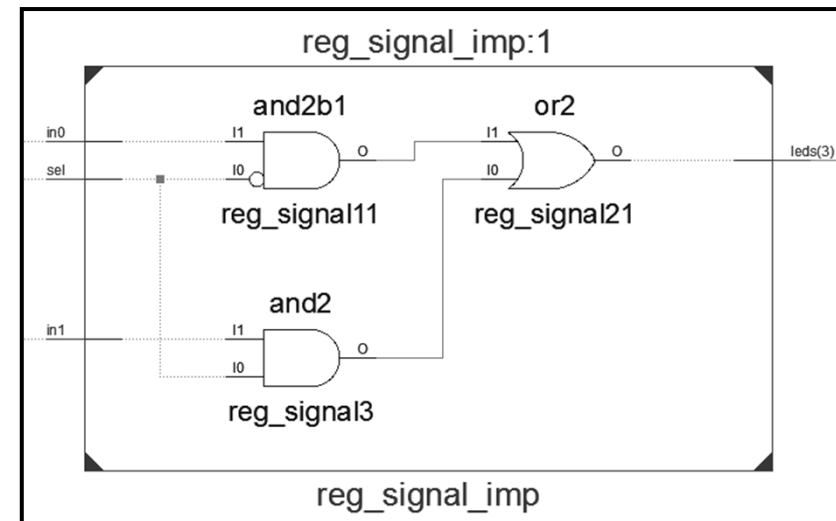
# Implementing combinational logic

- Latches are undesired, they implement asynchronous sequential logic and not combinational logic
- When the IF/CASE instructions are fully specified (IF: all else paths are present, CASE: all possible alternatives are listed or the default keyword is used):
  - The result will be combinational logic (example: MUX)

```
reg reg_signal;  
  
always @(*)  
    if (sel)  
        reg_signal <= in1;  
    else  
        reg_signal <= in0;
```




# Implementing sequential logic

- Only reg type signals can implement sequential logic:
  - Asynchronous: latches (**must be avoided !**)
  - Synchronous: flip-flops, registers
- Registers change their state at the rising or falling edge of the clock signal
  - The sensitivity list of the always block must contain the clock signal preceded by the **posedge** (rising edge) or the **negedge** (falling edge) keyword
- The IF/CASE instructions can be not fully specified
  - If so, the clock enable input of the flip-flops is used to prevent the state change when there is no assignment


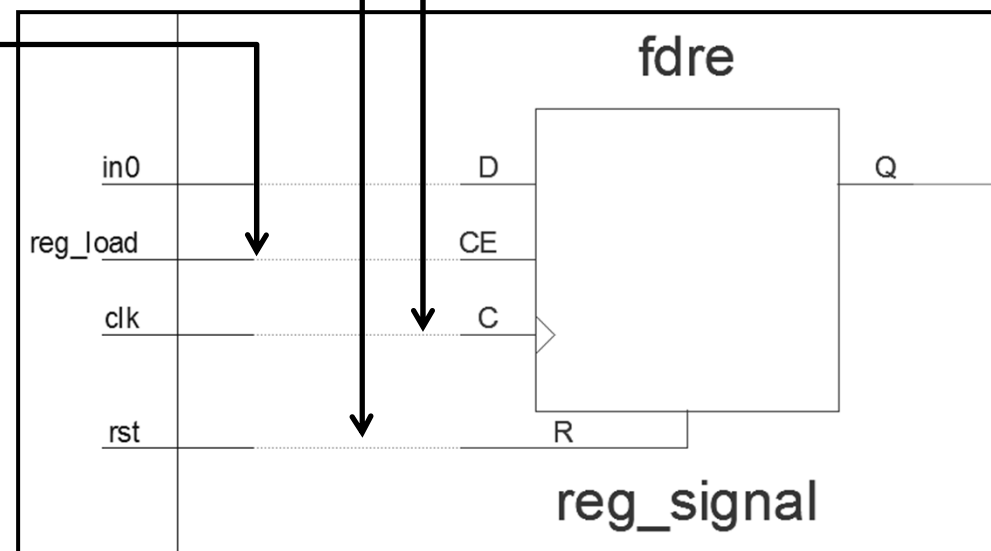
# Implementing sequential logic

```
reg reg_signal;  
always @(posedge clock  
         clk)  
    if (rst)  
        reg_signal <= 1'b0;  
    else clock enable  
        if (reg_load)  
            reg_signal <= in0;
```



# Datapath components

- **Adder:**

- Use the + operator
- The result is 1 bit wider: MSb is the carry out

```
wire [15:0] a, b, sum;  
wire      cin, cout;  
assign {cout, sum} = a + b + cin;
```

- **Subtractor:**

- Use the - operator
- The result is 1 bit wider: MSb is the borrow out
- No borrow input

```
wire [15:0] a, b, diff;  
wire      bout;  
assign {bout, diff} = a - b;
```

- **Adder/subtractor:**

```
wire [15:0] a, b;  
wire [16:0] result; //result[16]: carry/borrow output  
wire      sel;  
assign result = (sel) ? (a - b) : (a + b);
```



# Datapath components

- **Shifter:**

- Use the { } (concatenation) operator instead of the shift operators
- Specifying the bit length of the constants is necessary

```
wire [7:0] din;  
wire [7:0] lshift = {din[6:0], 1'b0}; //left shift  
wire [7:0] rshift = {1'b0, din[7:1]}; //right shift
```

- **Comparator:**

- Use the relational operators

```
wire [15:0] a, b;  
wire          a_lt_b = (a < b);    //lower than cmp.  
wire          a_eq_b = (a == b);   //equality cmp.  
wire          a_gt_b = (a > b);    //greater than cmp.
```

- **Multiplier:**

- Use the \* operator
- The bit length of the product is the sum of the bit length of the inputs
- Can be synthesized only if the FPGA contains multipliers

```
wire [15:0] a, b;  
wire [31:0] prod = a * b;
```



# Datapath components

- **Shift register (example):**
  - Synchronous reset and load
  - Bi-directional: left and right shift

```
reg [7:0] shr;
wire [7:0] din;
wire      rst, load, dir, serin;

always @(posedge clk)
    if (rst)
        shr <= 8'd0;                //reset
    else
        if (load)
            shr <= din;              //load
        else
            if (dir)
                shr <= {serin, shr[7:1]}; //right shift
            else
                shr <= {shr[6:0], serin}; //left shift
```

# Datapath components

- **Counter (example):**

- Synchronous reset and load
- Bi-directional: up/down counter

```
reg [8:0] cnt;
wire [8:0] din;
wire      rst, load, dir;
wire      tc = (dir) ? (cnt==9'd0) : (cnt==9'd511);

always @(posedge clk)
    if (rst)
        cnt <= 9'd0;                //reset
    else
        if (load)
            cnt <= din;              //load
        else
            if (dir)
                cnt <= cnt - 9'd1;    //down count
            else
                cnt <= cnt + 9'd1;    //up count
```

# Priority of the control signals

- The value of the control inputs are examined in the order they are listed in the always block
- The reset signal should have the highest priority (should be the first)
- Wrong logic may be synthesized if the order of the control inputs is not what the development tool expects

```
always @(posedge clk)
  if (rst)
    cnt <= 9'd0;
  else
    if (load)
      cnt <= data_in;
    else
      if (en)
        cnt <= cnt + 9'd1;
```

rst	load	en	Operation
1	x	x	Reset
0	1	x	Load
0	0	1	Up count
0	0	0	No change

```
always @(posedge clk)
  if (rst)
    cnt <= 9'd0;
  else
    if (en)
      if (load)
        cnt <= data_in;
      else
        cnt <= cnt + 9'd1;
```

rst	en	load	Operation
1	x	x	Reset
0	1	1	Load
0	1	0	Up count
0	0	x	No change

# Synchronous/asynchronous control signals

- Synchronous control signals:

- Have effect only at the rising or falling clock edge
- The sensitivity list doesn't contain the synchronous control signals

```
//Active high sync. reset
always @(posedge clk)
    if (rst)
        some_reg <= 1'b0;
    else
        some_reg <= data_in;
```

```
//Active low sync. reset
always @(posedge clk)
    if (rst == 0)
        some_reg <= 1'b0;
    else
        some_reg <= data_in
```

- Asynchronous control signals

- Have immediate effect
- The sensitivity list must contain the asynchronous control signals preceded with the **posedge** or the **negedge** keyword


```
//Active high async. reset
always @(posedge clk, posedge rst)
    if (rst)
        some_reg <= 1'b0;
    else
        some_reg <= data_in;
```

```
//Active low async. reset
always @(posedge clk, negedge rst)
    if (rst == 0)
        some_reg <= 1'b0;
    else
        some_reg <= data_in
```


 
# Finite state machines (FSMs)

- **Local parameters can be used to define the states**
- **A register is required to store the current state**
- **The CASE instruction can be used to select the current state**
  - In each alternative, the IF or CASE instructions can be used to check the value of the inputs and execute the proper state transition
- **Example: traffic light controller**
  - 4 states: red, red-yellow, green, yellow
  - An external timer generates the 1 clock cycle long enable signal



# Finite state machines (FSMs)

- **1st implementation:**
  - The state register and the next state logic are in the same always block
  - User state encoding

```
localparam STATE_R = 2'd0;
localparam STATE_RY = 2'd1;
localparam STATE_G = 2'd2;
localparam STATE_Y = 2'd3;

reg [1:0] state;

//State register and the next state logic
always @(posedge clk)
begin
    if (rst)
        state <= STATE_R;
    else
        case (state)
            STATE_R : if (enable)
                        state <= STATE_RY;
                    else
                        state <= STATE_R;
        endcase
end
```

```
STATE_RY: if (enable)
    state <= STATE_G;
else
    state <= STATE_RY;
STATE_G : if (enable)
    state <= STATE_Y;
else
    state <= STATE_G;
STATE_Y : if (enable)
    state <= STATE_R;
else
    state <= STATE_Y;

endcase
end

//Driving the outputs
assign r = (state==STATE_R) | (state==STATE_RY);
assign y = (state==STATE_Y) | (state==STATE_RY);
assign g = (state==STATE_G);
```

# Finite state machines (FSMs)

- **2nd implementation:**

- The state register and the next state logic are in different always blocks
- User state encoding

```
localparam STATE_R  = 2'd0;
localparam STATE_RY = 2'd1;
localparam STATE_G  = 2'd2;
localparam STATE_Y  = 2'd3;

reg [1:0] current_state;
reg [1:0] next_state;

//State register (sequential logic)
always @(posedge clk)
    if (rst)
        current_state <= STATE_R;
    else
        if (enable)
            current_state <= next_state;
```

```
//Next state logic (combinational logic)
always @(*)
    case (current_state)
        STATE_R : next_state <= STATE_RY;
        STATE_RY: next_state <= STATE_G;
        STATE_G : next_state <= STATE_Y;
        STATE_Y : next_state <= STATE_R;
    endcase

//Driving the outputs
assign r = (current_state == STATE_R) |
          (current_state == STATE_RY);
assign y = (current_state == STATE_Y) |
          (current_state == STATE_RY);
assign g = (current_state == STATE_G);
```

# Finite state machines (FSMs)

- **3rd implementation:**

- The state register and the next state logic are in different always blocks
- Output encoding: the (\* fsm\_encoding = "user" \*) **Xilinx-specific** Verilog directive disables the state encoding optimization for the state register

```
localparam STATE_R  = 3'b100;
localparam STATE_RY = 3'b110;
localparam STATE_G  = 3'b001;
localparam STATE_Y  = 3'b010;

(* fsm_encoding = "user" *)
reg [2:0] current_state;
reg [2:0] next_state;

//State register (sequential logic)
always @(posedge clk)
    if (rst)
        current_state <= STATE_R;
    else
        if (enable)
            current_state <= next_state;
```

```
//Next state logic (combinational logic)
always @(*)
    case (current_state)
        STATE_R : next_state <= STATE_RY;
        STATE_RY: next_state <= STATE_G;
        STATE_G : next_state <= STATE_Y;
        STATE_Y : next_state <= STATE_R;
    endcase

//Driving the outputs
assign r = current_state[2];
assign y = current_state[1];
assign g = current_state[0];
```



# Memories (RAMs, ROMs)

- **Verilog description of the memories:**
  - Memories can be treated as a one-dimensional array
    - WIDTH: number of bits in a data word
    - WORDS: number of data words in the memory, this value must be a power of 2
  - Memories store data therefore the array must be declared as a register type



```
reg [WIDTH-1:0] mem [WORDS-1:0];
```

- **Xilinx FPGAs contain two different memory resources**
  - Distributed RAM
  - Block RAM


  
# Memories (RAMs, ROMs)

- **Distributed RAM:**
  - Useful for storing small amount of data (for example: register file)
  - 1 write port and 1 or 2 read port(s)
    - The address is shared between the write and the first read port (**A**)
    - The address for the second read port can be different (**DPRA**)
  - Write is synchronous
    - Happens at the rising (or falling) clock edge when the write enable is high
  - Read is asynchronous
    - Read data appears immediately on the data output



# Memories (RAMs, ROMs)

- Verilog description of the distributed RAM:
  - Example: 32 x 4 bit RAM with 1 write and 2 read ports
  - The (\* ram\_style = "distributed" \*) **Xilinx-specific** Verilog directive instructs the development tool to use distributed RAM for this memory

```
(* ram_style = "distributed" *)
reg  [3:0] mem [31:0];
wire [4:0] addr_a;      //Address for write and 1st read port
wire [4:0] addr_b;      //Address for the 2nd read port
wire [3:0] din;         //Input data
wire      write_en;     //Write enable signal

//Write port (synchronous)
always @(posedge clk)
    if (write_en)
        mem[addr_a] <= din;



//Read ports (asynchronous)
wire [3:0] dout_a = mem[addr_a];
wire [3:0] dout_b = mem[addr_b];
```


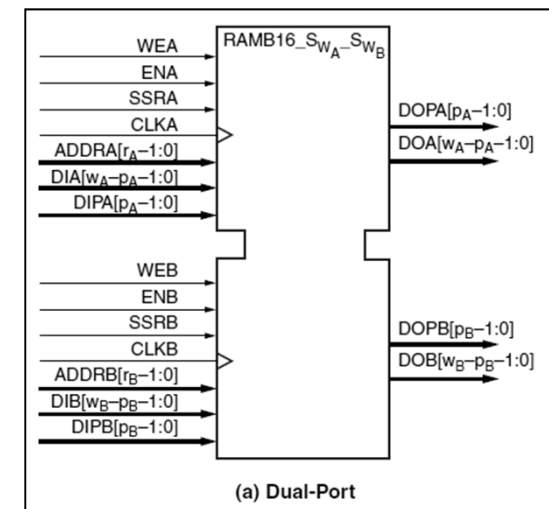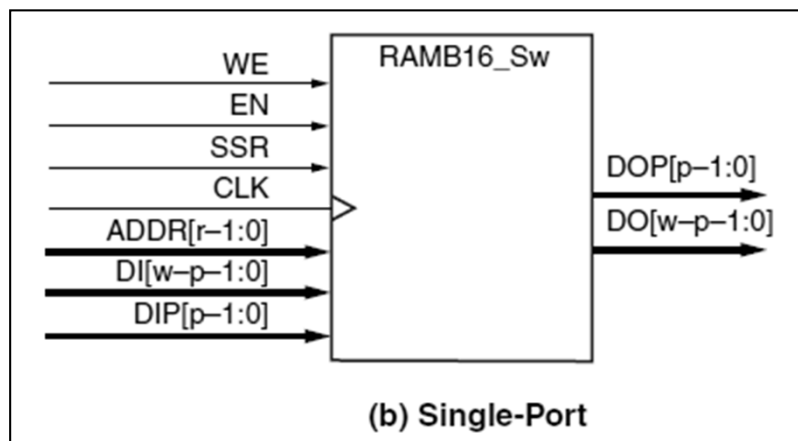
# Memories (RAMs, ROMs)

- **Block RAM:**

- 18 kbit capacity per RAM block, different configurations
  - 16k x 1 bit, 8k x 2 bit, 4k x 4 bit, 2k x 9 bit, 1k x 18 bit and 512 x 36 bit
- Dual-port memory: two independent read/write ports (x = A,B)
  - Clock (**CLKx**), data output reset (**SSRx**), enable (**ENx**), write enable (**WEx**),
  - Address input (**ADDRx**), data input (**DIx, DIPx**), data output (**DOx, DOPx**)
- Write and read is synchronous
  - Write happens at the rising (or falling) clock edge when **ENx=1** and **WEx=1**
  - Read happens at the rising (or falling) clock edge when **ENx=1**
  - **Synchronous read: 1 clock cycle read delay!**



# Memories (RAMs, ROMs)

- **Verilog description of the Block RAM:**
  - Example: 2k x 12 bit RAM with 1 write and 1 read ports
  - The (\* ram\_style = "block" \*) **Xilinx-specific** Verilog directive instructs the development tool to use Block RAM for this memory

```
(* ram_style = "block" *)
reg  [11:0] mem [2047:0];
wire [10:0] wr_addr;      //Address for write port
wire [10:0] rd_addr;      //Address for read port
wire [11:0] din;          //Input data
reg  [11:0] dout;         //Output data (sync. read -> reg type!)
wire          write_en;   //Write enable signal

//Write and read ports (synchronous)
always @(posedge clk)
begin
    if (write_en)
        mem[wr_addr] <= din;
    dout <= mem[rd_addr];
end
```



# Memories (RAMs, ROMs)

- **Initializing the RAM contents via an external data file:**

- The data file must contain a binary or hexadecimal string per line
- The number of lines in the data file must be equal with the number of words in the RAM
- Use the ***\$readmemb*** (binary data file) or ***\$readmemh*** (hexadecimal data file) Verilog functions inside an ***initial*** block

```
$readmemb("data_file", ram_name, start_addr, end_addr);  
$readmemh("data_file", ram_name, start_addr, end_addr);
```

- **Initial blocks:**

**initial**

**assignments**

- Cannot be used for implementing hardware components
- The assignments in the initial block are evaluated at the beginning of the synthesis or the simulation
- **if...else** and **case** instructions can be used in initial blocks
- Multiple statements must be grouped using **begin** and **end** keywords



# Memories (RAMs, ROMs)

- **Example: initializing the contents of the 2k x 12 bit RAM**

```
(* ram_style = "block" *)
reg  [11:0] mem [2047:0];
wire [10:0] wr_addr;      //Address for write port
wire [10:0] rd_addr;      //Address for read port
wire [11:0] din;          //Input data
reg  [11:0] dout;          //Output data (sync. read -> reg type!)
wire          write_en;    //Write enable signal

//Initializing the RAM contents
initial
    $readmemh("mem_data_hex.txt", mem, 0, 2047);

//Write and read ports (synchronous)
always @(posedge clk)
begin
    if (write_en)
        mem[wr_addr] <= din;
    dout <= mem[rd_addr];
end
```



# Memories (RAMs, ROMs)

- **Small ROMs can be described using the case instruction:**

```
wire [2:0] rom_addr;    // 8 x 8 bit ROM
reg  [7:0] rom_dout;
```

```
always @(*)
  case (rom_addr)
    3'd0: rom_dout <= 8'b1010_1010;
    3'd1: rom_dout <= 8'b1111_1000;
    3'd2: rom_dout <= 8'b0010_0000;
    3'd3: rom_dout <= 8'b1110_0011;
    3'd4: rom_dout <= 8'b0000_0000;
    3'd5: rom_dout <= 8'b0010_1110;
    3'd6: rom_dout <= 8'b1011_1011;
    3'd7: rom_dout <= 8'b1111_1011;
  endcase
```

- **Without the write port, the distributed RAMs and the Block RAMs can be used as ROMs**
  - The contents of the ROM must be initialized





# Memories (RAMs, ROMs)

- Verilog description of the distributed ROM:
  - Example: 32 x 4 bit ROM
  - The (\* rom\_style = "distributed" \*) Xilinx-specific Verilog directive instructs the development tool to use distributed ROM for this memory

```
(* rom_style = "distributed" *)
reg  [3:0] mem [31:0];
wire [4:0] rd_addr;      //Read address
wire [3:0] dout          //Output data

//Initializing the ROM contents
initial
    $readmemh("rom_data_hex.txt", mem, 0, 31);

//Read port (asynchronous)
wire [3:0] dout = mem[rd_addr];
```



# Memories (RAMs, ROMs)

- Verilog description of the Block ROM:
  - Example: 2k x 12 bit ROM with 2 read ports
  - The (\* rom\_style = "block" \*) **Xilinx-specific** Verilog directive instructs the development tool to use Block RAM for this ROM

```
(* rom_style = "block" *)
reg  [11:0] mem [2047:0];
wire [10:0] rd_addr1;      //Address for the first read port
wire [10:0] rd_addr2;      //Address for the second read port
reg  [11:0] dout1;         //Output data (sync. read -> reg type!)
reg  [11:0] dout2;         //Output data (sync. read -> reg type!)

//Initializing the ROM contents
initial
    $readmemh("rom_data_hex.txt", mem, 0, 2047);

//Read ports (synchronous)
always @(posedge clk)
begin
    dout1 <= mem[rd_addr1];
    dout2 <= mem[rd_addr2];
end
```

# Three-state drivers

- Three state drivers are only available for the I/O pins of the FPGA device
- Internal signals cannot be high-impedance
- Verilog description of the three-state drivers


- Output pin

```
output wire [7:0] dout_pin;
```

```
wire [7:0] data_out;
```

```
wire      oe;
```
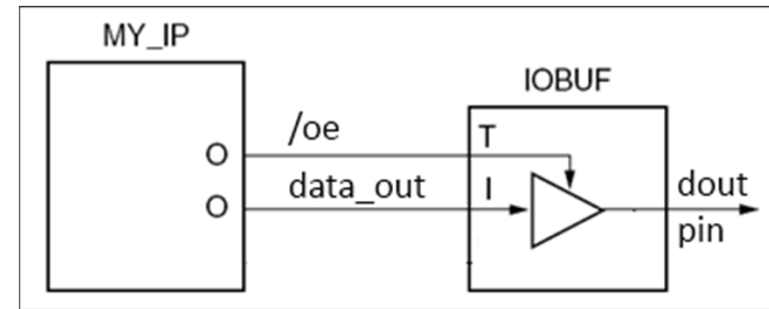
```
assign dout_pin = (oe) ? data_out : 8'bzzzz_zzzz;
```



- Bi-directional (I/O) pin

```
inout wire [7:0] bidir_pin;
```

```
wire [7:0] data_out;
```

```
wire [7:0] data_in;
```

```
wire      oe;
```

```
assign bidir_pin = (oe) ? data_out : 8'bzzzz_zzzz;
```

```
assign data_in    = bidir_pin;
```

